


Mathematics 1E2 2006–07
HW 15 Due 26/2/07

Name: _____
 ID: _____

(1)(12 marks) Show by tables that (i) $X \implies Y$ and $Y \implies X$ are not equivalent, but (ii) $X \implies Y$ and $(\neg Y) \implies (\neg X)$ are equivalent.


(2)(8 marks) Complete the truth-table for circuit (i) below.

X	Y	$f(X, Y)$
0	0	
0	1	
1	0	
1	1	

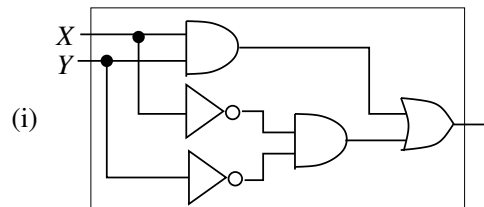

(3) (16 marks) and for circuit (ii):

X	Y	Z	$f(X, Y, Z)$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

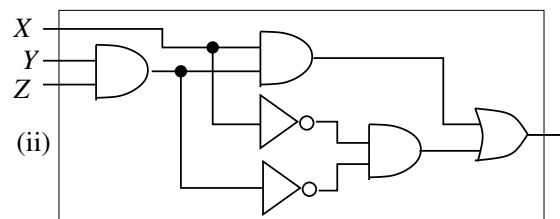

(4)(14 marks) Construct an expression, using only \implies and \neg , which realises the function computed by circuit (ii) above. **Show the construction in steps; otherwise it can't be followed.**