

Mathematics 1E2 2006–07
HW 16 Due 5/3/07


Name: _____
 ID: _____

(1)(16 marks) Prove by resolution that the CNF

$$ABC, \overline{A}BC, A\overline{B}C, B\overline{C}, \overline{A}BC, \overline{A}\overline{B}$$

is inconsistent.

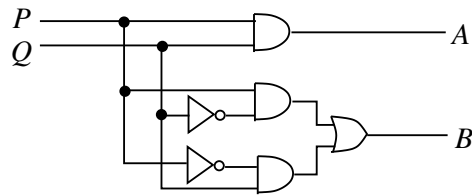(2) (16 marks) Construct a truth-table (with columns for inputs P, Q and outputs A, B). Hence say what it does.



(3)(18 marks) Using the 3-bit addition circuit as a starting-point, design a circuit which converts input $P_2P_1P_0$ to its 2s complement, by negating all bits and adding 1.